


## of Transmission Cables in Charging Applications

## Circuit Simulation

D.K.M.A.M. Padmal - 140427D
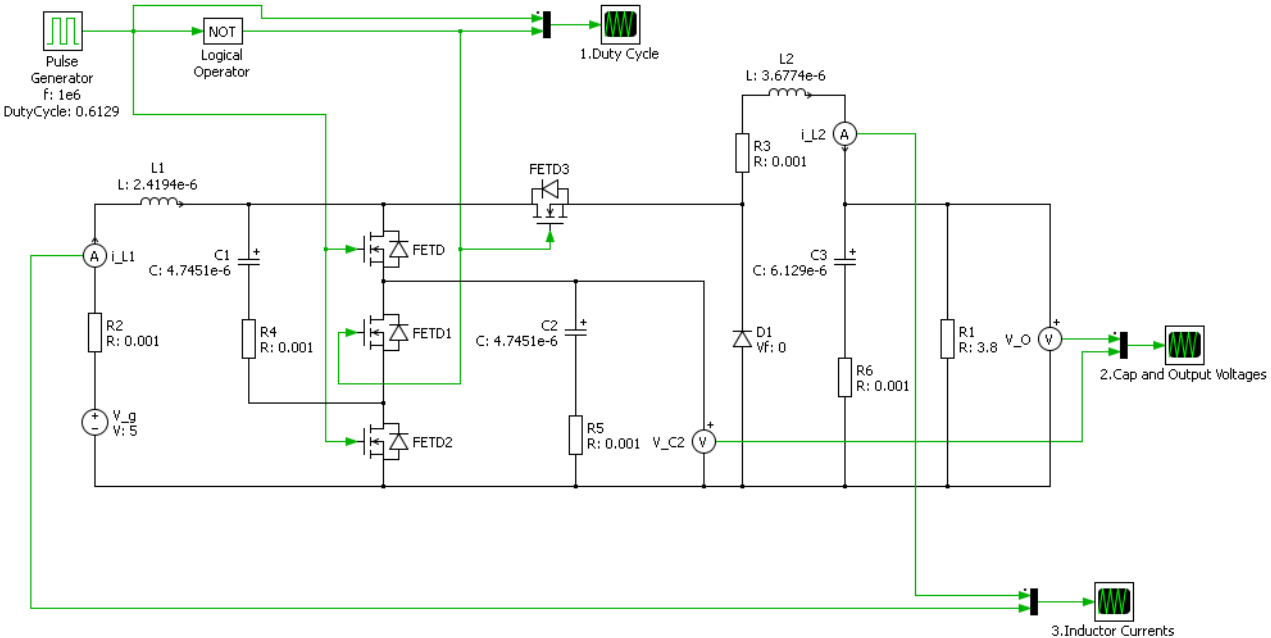
# 1 Circuit

The circuit simulations in this report were done with the following circuit created using PLECS



## 2 Parameters


Following parameters were used in the circuit simulation

Component	Simulated Values
Source Voltage ( $V_g$ )	5 V
Duty Ratio ( $D$ )	0.6129
Load Resistance ( $R_o$ )	3.8 $\Omega$
Output Voltage ( $V_o$ )	3.8 V
Switching Frequency ( $f_s$ )	1 MHz
Inductor ( $L_1$ )	2.4194 $\mu$ H, ESR = 0.001 $\Omega$
Inductor ( $L_2$ )	3.6774 $\mu$ H, ESR = 0.001 $\Omega$
Capacitor ( $C_1, C_2$ )	4.7451 $\mu$ F, ESR = 0.001 $\Omega$
Capacitor ( $C_o$ )	6.1290 $\mu$ F, ESR = 0.001 $\Omega$

## 3 Simulations
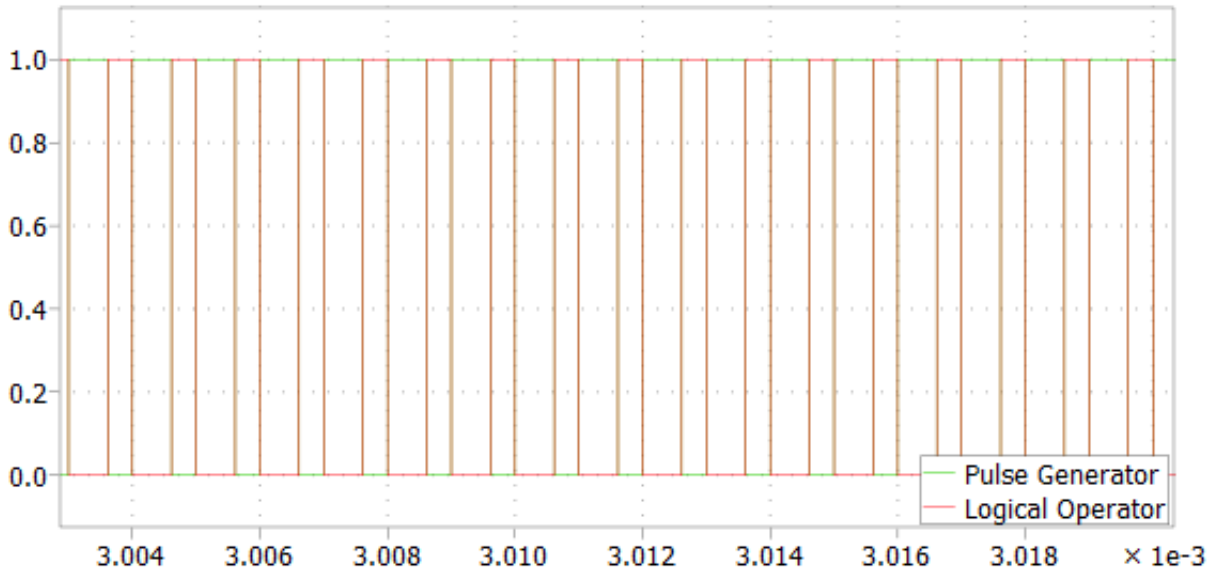
### 3.1 Duty Cycle

Pulse generator is used to generate the square wave to drive the MOSFETs and the following waveform is observed.



## 3.2 Output Voltage Waveforms

Output voltage waveform is observed across the  $R_o$  resistor and an intermediate waveform can be observed across the  $C_1$  or  $C_2$  capacitor.

Figure 1: Output Voltage Waveform


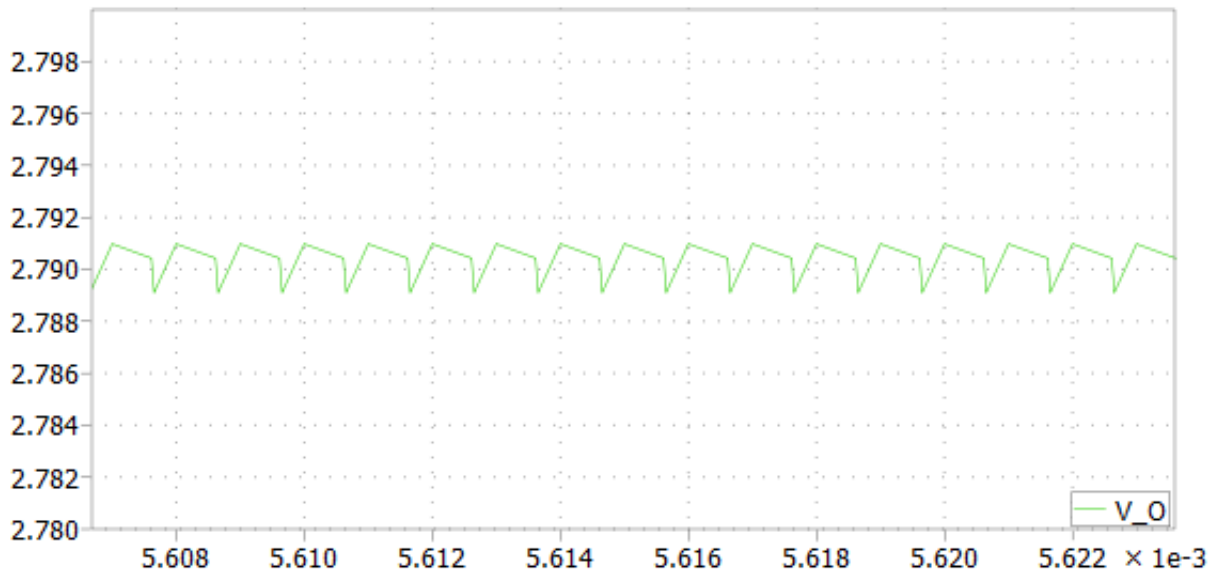



Figure 2: Capacitor Voltage Waveform

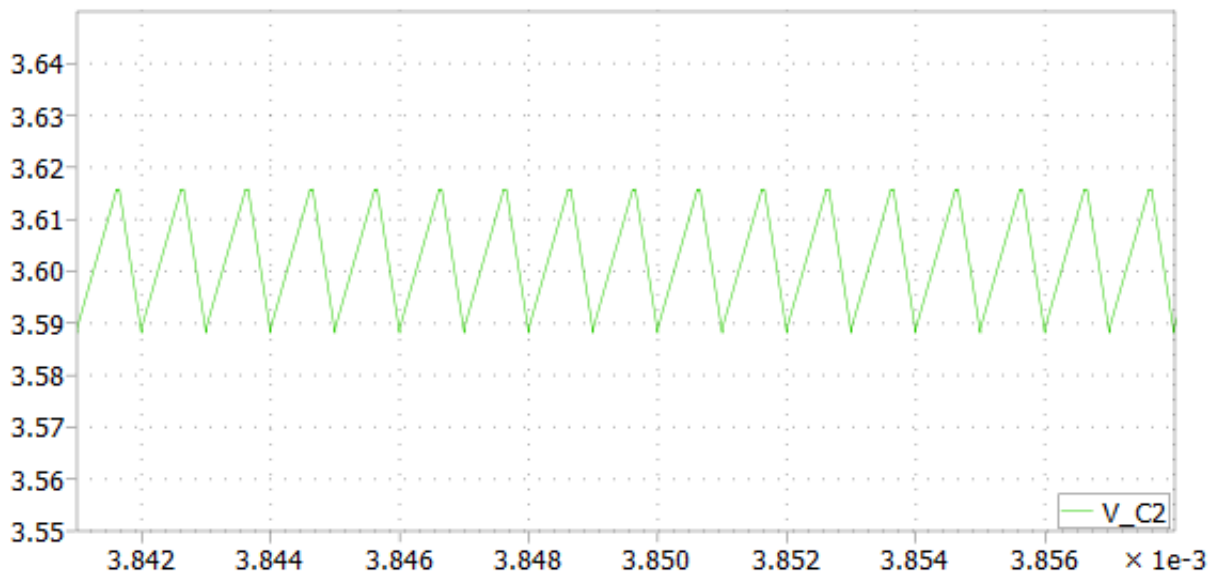

### 3.3 Inductor Current Waveforms

Current across the inductors  $L_1$  and  $L_2$  were observed as follows;

Figure 3: Inductor Current Waveforms

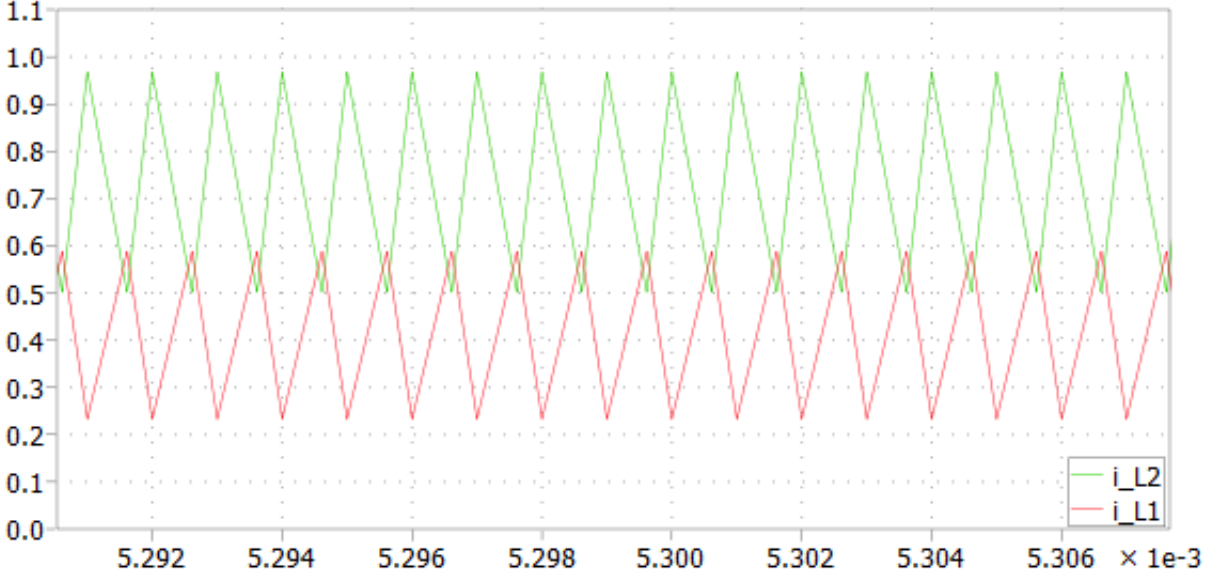

## 4 Voltage Gain

Output voltage expression was derived as follows;

$$V_o = \frac{2DV_g - (1 + D)V_{D1}D'}{(1 + D) + \frac{R_Z}{R_o}}$$

By dividing both sides by  $V_g$  we can derive the voltage gain function for non ideal case.

$$\frac{V_o}{V_g} = \frac{2D - (1 + D)\frac{V_{D1}}{V_g}D'}{(1 + D) + \frac{R_Z}{R_o}}$$

This will simplify into;

$$M = \frac{2D}{(1 + D) + \frac{R_Z}{R_o}} - \frac{(1 + D)\frac{V_{D1}}{V_g}D'}{(1 + D) + \frac{R_Z}{R_o}}$$

There is another step taken in the plots. That is when the diode forward voltage is zero and when it is 0.6 V.

For both ideal and non-ideal cases, gain function can be plotted as follows;

Figure 4: Gain Plots when  $V_f = 0$  V


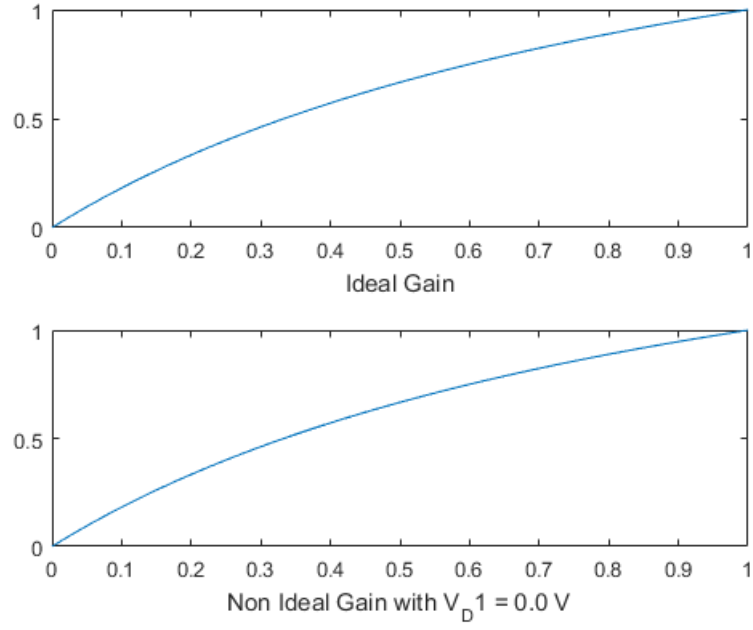


Figure 5: Gain Plots when  $V_f = 0.6$  V

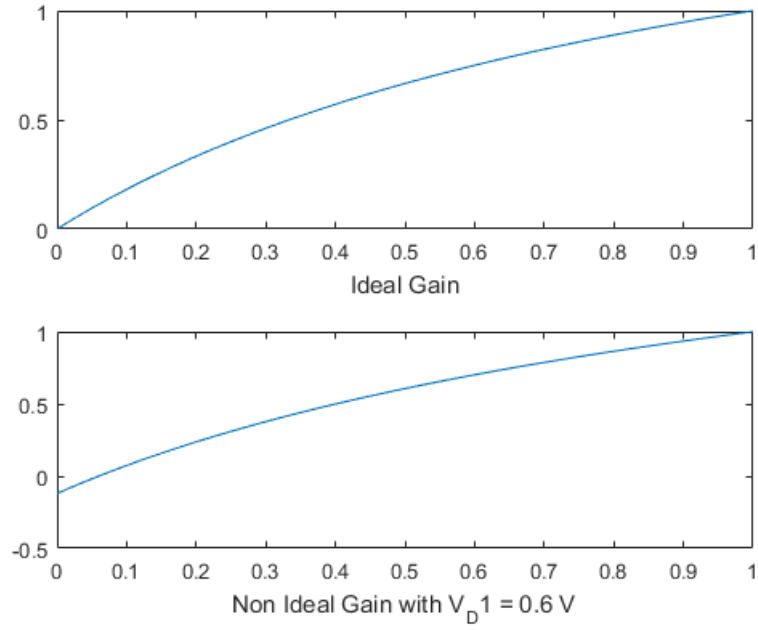

## 5 Transfer Functions

There are two transfer functions taken into consideration at four different input parameters.

## 5.1 Line to Output Transfer Function

Line to Output transfer function ( $G_{vg}(s)$ ) is expressed as;

$$G_{vg}(s) = \frac{(1 + D)}{2D} \frac{u(s)}{z(s)}$$

Where;

$$z(s) = \frac{R_o + (L_a + L_2)s + (L_a C_o + L_a C_a + L_2 C_o)R_o s^2 + L_a L_2 C_a s^3 + L_a C_a L_2 C_o R_o s^4}{1 + R(C_a + C_o) + L_2 C s^2 + L_2 C_o C R_o S^3}$$

$$u(s) = \frac{R_o}{1 + R_o C_o s}$$

$$L_a = \frac{4D^2}{(1 + D)^2} L_1$$

$$C_a = \frac{C}{D^2}$$

## 5.2 Control to Output Transfer Function

Control to Output transfer function ( $G_{vd}(s)$ ) is expressed as;

$$G_{vd}(s) = e(s) \frac{(1+D)}{2D} \frac{u(s)}{z(s)}$$

Where;

$$z(s) = \frac{R_o + (L_a + L_2)s + (L_a C_o + L_a C_a + L_2 C_o)R_o s^2 + L_a L_2 C_a s^3 + L_a C_a L_2 C_o R_o s^4}{1 + R(C_a + C_o) + L_2 C s^2 + L_2 C_o C R_o s^3}$$

$$u(s) = \frac{R_o}{1 + R_o C_o s}$$

$$L_a = \frac{4D^2}{(1+D)^2} L_1$$

$$C_a = \frac{C}{D^2}$$

## 5.3 Source Code

### 5.3.1 Gain Plots

```
1 % Duty Cycle
2 D = 0:0.001:1;
3 d = 1 - D;
4 % Ideal Condition
5 IdealGain = 2 * D ./ (1 + D);
6
7 % Non Ideal Condition
8 V_D1 = 0.6;
9 V_g = 5;
10 R_L1 = 0.001;
11 R_L2 = 0.001;
12 R_C1 = 0.001;
13 R_C2 = 0.001;
14 R_o = 3.8;
15
16 % On resistance of semiconductors are assumed to be zero , therefore
17 R_Z = (1 + D) .* R_L2 + (D / (1 + D)) .* (4 * D .* R_L1 + d .* (R_C1 +
    R_C2));
18
19 First_Term = 2 * D ./ (1 + D + (R_Z / R_o));
20 Second_Term = - ((1 + D) .* (V_D1 / V_g) .* d) ./ (1 + D + (R_Z / R_o))
    ;
21 NonIdealGain = (First_Term + Second_Term);
22
23 figure
24 subplot(2,1,1);
25 plot(D,IdealGain);
26 xlabel('Ideal Gain');
27
28 subplot(2,1,2);
29 plot(D,NonIdealGain);
30 xlabel('Non Ideal Gain with V_D1 = 0.6 V');
```

### 5.3.2 Transfer Functions


```
1 % Duty Cycle
2 D = 0.6129;
3
4 % Passive component values
5 R_o = 3.8;
6 C_o = 6.1290e-6;
7 C_c = 4.7451e-6;
8 L_1 = 2.4194e-6;
9 L_2 = 3.6774e-6;
```




```

10 V_o = 3.3;
11
12 V_g = V_o * (1 + D) / (2 * D);
13 I_o = 1;
14
15 % Derived parameters
16 I_g = I_o * 2 * D / (1 + D); %
17 L_a = L_1 * ((4 * (D ^ 2)) / ((1 + D) ^ 2)); %
18 C_a = C_c / (D ^ 2); %
19 D_fac = 1 / (D + D ^ 2); %
20
21 % Intermediate transfer functions
22 U_S = tf(R_o, [(R_o * C_o), 1]); %
23 Z_S = tf([(L_a * C_a * L_2 * C_o * R_o), (L_a * L_2 * C_a), (R_o * (L_a
    * C_o + L_a * C_a + L_2 * C_o)), (L_a + L_2), R_o], [(L_2 * C_o *
    C_a * R_o), (L_2 * C_a), ((C_a + C_o) * R_o + 1)]); %
24 E_S = tf([(-4 * L_1 * V_g * C_c * D_fac / (1 + D)), (L_1 * I_g * D_fac)
    , (-D * V_g * D_fac)], 1); %
25
26 % Transfer Functions
27 G_vg = ((1 + D) * U_S) / (2 * D * Z_S);
28 G_vd = ((1 + D) * U_S * 1) / (2 * D * Z_S);
29 bode(G_vd);
30 xlabel('G_vd(s) at V_o = 3.3 V and I_o = 1 A');
31 grid


```

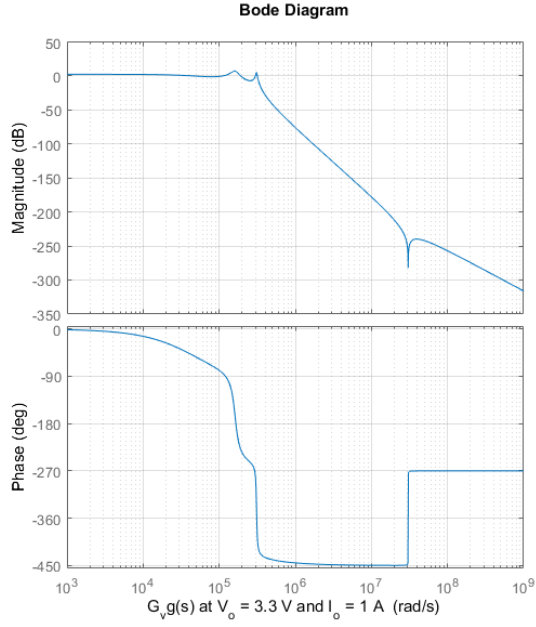

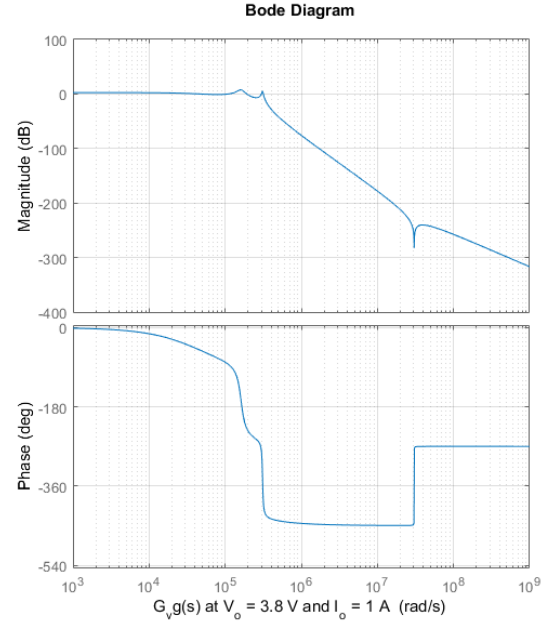
(a)  $G_{vg}(s)$  when  $V_o = 3.3$  V and  $I_o = 1$  A



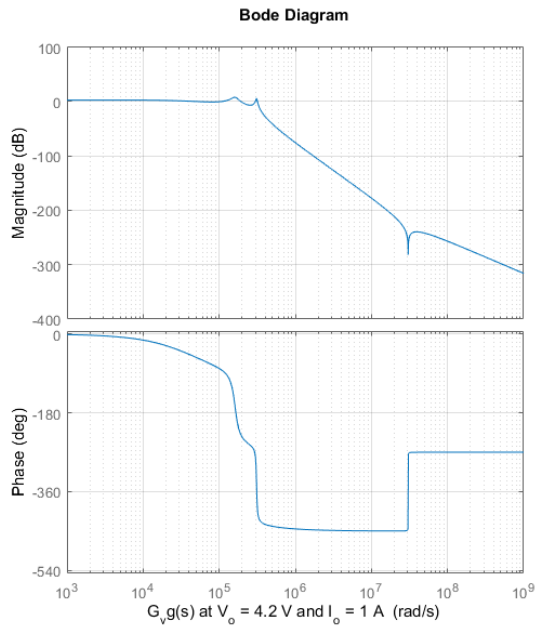
(b)  $G_{vg}(s)$  when  $V_o = 3.8$  V and  $I_o = 1$  A



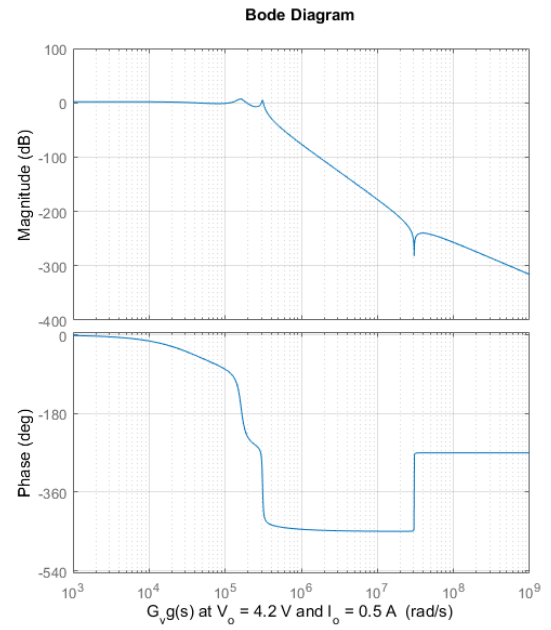
(c)  $G_{vg}(s)$  when  $V_o = 4.2$  V and  $I_o = 1$  A



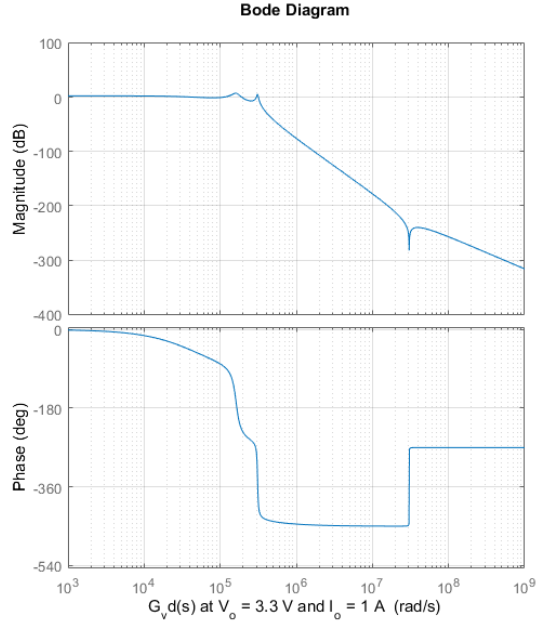
(d)  $G_{vg}(s)$  when  $V_o = 4.2$  V and  $I_o = 0.5$  A



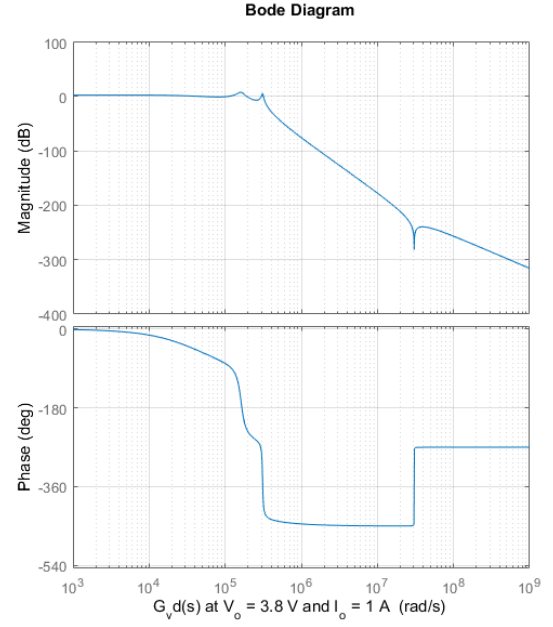
(a)  $G_{vd}(s)$  when  $V_o = 3.3\text{V}$  and  $I_o = 1\text{A}$



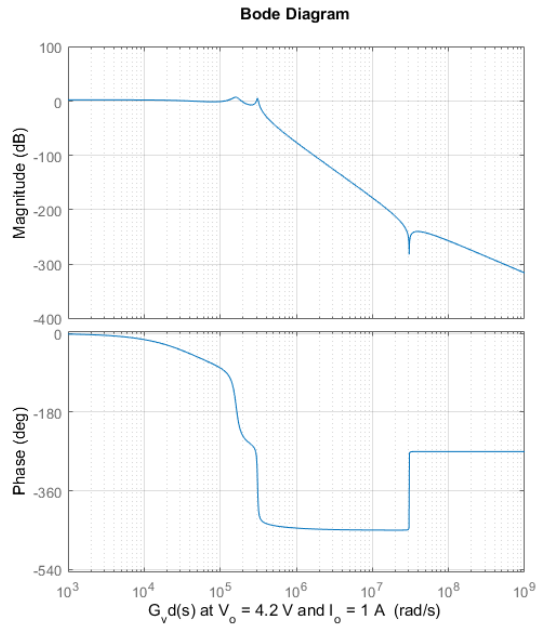(b)  $G_{vd}(s)$  when  $V_o = 3.8\text{V}$  and  $I_o = 1\text{A}$



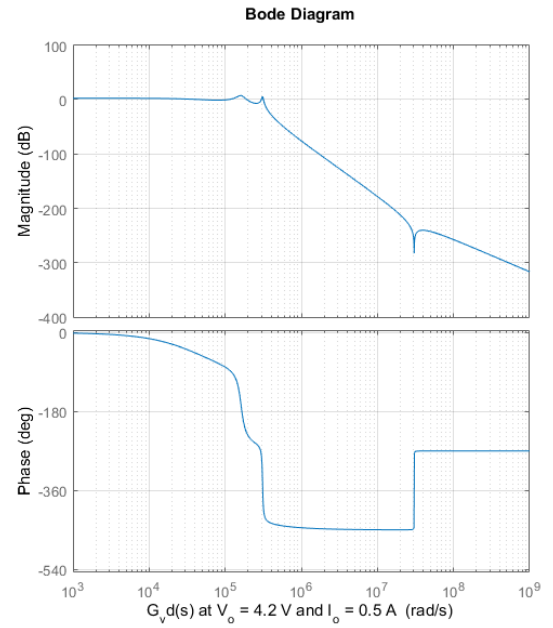(c)  $G_{vd}(s)$  when  $V_o = 4.2\text{V}$  and  $I_o = 1\text{A}$



(d)  $G_{vd}(s)$  when  $V_o = 4.2\text{V}$  and  $I_o = 0.5\text{A}$